

Temperature Compensation Circuit for Constant LED Intensity

Application Brief I-012

Introduction

The luminous intensity of an LED has a temperature dependence of $\exp [k (T - T_A)]$ where k is on the order of $-0.01 / ^\circ\text{C}$. This means that as temperature linearly increases or decreases, the light intensity of an LED exponentially decreases or increases respectively. This characteristic is a liability in outdoor applications where the LED becomes dimmer during the warmer daytime when sunlight visibility is of concern. The circuit configuration shown in Figure 1 is an example of how to minimize the intensity dependency on temperature problems in a voltage sourced application where the LED current is set with the LED in series with a current limiting resistor (R_{lim}). This configuration can also be used as a discrete circuit whose output is referred to other LED biasing networks (that have the same type of LED as the discrete) under the same ambient temperature condition.

Description

If large enough quiescent voltage levels (i.e. $V_b < -5$ Volts) are used to bias the LED under nominal temperature conditions, then any pn junction potential variations (i.e. silicon = $-2 \text{ mV}/^\circ\text{C}$ is a small linear value) can be treated as negligible in a circuit trying to compensate for the exponential dependence of light intensity on temperature.

The circuit in Figure 1 utilizes a temperature compensated current source feeding a PIN photo-diode and a transresistance amplifier. The transresistance amplifier's output drives the base of a PNP transistor used to supply voltage and current to the LED and current limiting resistor. The details of designing each part of the circuit are not the scope of this application brief as much as is the concept of the overall circuit's functionality.

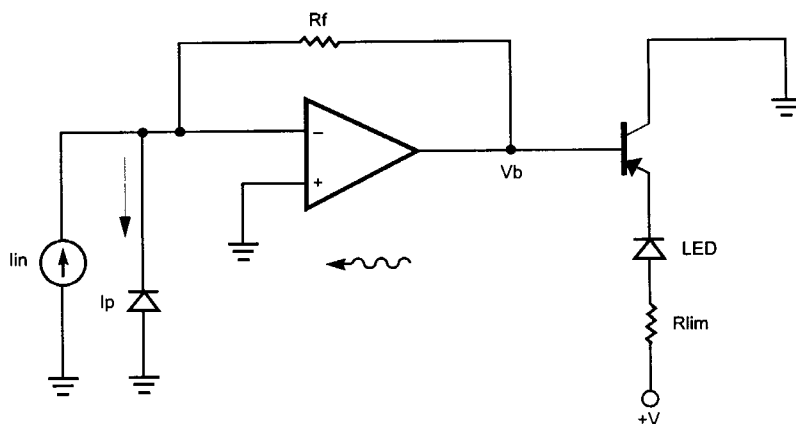


Figure 1. Temperature Compensation Circuit for Constant LED Intensity.

As a cause and effect example, compensation for an increase in temperature will be described here. As the temperature increases, the nominal light intensity of the LED will decrease. This decreases the amount of light falling on the photodiode and thus decreases the photodiode current. However, this effect increases the percentage of current I_{in} being fed through the feedback resistor R_f . This causes the base of the PNP to drop its voltage value and thus increase the LED current. Increasing the LED current increases the LED luminous intensity to near the nominal value. How stable the LED light intensity can be made with this circuit configuration will depend upon the nominal light output desired (the optical "Q" point) and the component values selected. It is important that the responsivity of the photodetector is high enough at the LED's dominant wavelength to allow for at least a few tens of microamps. If the responsivity is too low, then the current source value I_{in} will have to be low for the variations in the photodiode current to cause a significant change in the current flowing through the feedback resistor R_f . Working in the nanoamp region will be troublesome due to the combined inherent noise characteristics of all the components. Use as large a feedback resistor as possible with a low noise operational amplifier. Too large of an R_f value will not cause the feedback circuit to oscillate since the thermal transients are in the seconds range at best.

For product information and a complete list of distributors, please go to our web site: www.avagotech.com

Avago, Avago Technologies, and the A logo are trademarks of Avago Technologies, Limited in the United States and other countries. Data subject to change. Copyright © 2006 Avago Technologies Limited. All rights reserved.
5963-7544E - December 11, 2006

AVAGO
TECHNOLOGIES